

Period 2 Formulas

Series Circuits
$R_T = R_1 + R_2 + R_3 \dots$
$V_T = V_1 + V_2 + V_3 \dots$
$I_T = I_1 + I_2 + I_3 \dots$

Parallel Circuits
$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots$
$\frac{1}{V_T} = \frac{1}{V_1} + \frac{1}{V_2} + \frac{1}{V_3} \dots$
$\frac{1}{I_T} = \frac{1}{I_1} + \frac{1}{I_2} + \frac{1}{I_3} \dots$

Ohms Law
$E = I \times R$
$I = \frac{E}{R}$
$R = \frac{E}{I}$

Generator Formulas
$f = \frac{p \times n}{120}$
$p = \frac{f \times 120}{n}$

Power Formulas		
$P = I \times E$	$P = I^2 R$	$P = \frac{E^2}{R}$
$I = \frac{P}{E}$	$I = \sqrt{\frac{P}{R}}$	$R = \frac{E^2}{P}$
$E = \frac{P}{I}$	$R = \frac{P}{I^2}$	$E = \sqrt{P \times R}$

Trig Formulas
$\sin(\theta) = \frac{\text{opposite}}{\text{hypotenuse}}$
$\cos(\theta) = \frac{\text{adjacent}}{\text{hypotenuse}}$
$\tan(\theta) = \frac{\text{opposite}}{\text{adacent}}$

Power
$PF = 1 - \theta = 0^\circ$
$P = V \times I$
$P = \frac{V^2}{R}$
$P = I^2 \times R$

Inductance and Inductive Reactance

$$L = \frac{N^2 \mu A}{\ell}$$

Number of Turns → N
 Permeability of the Core → μ
 Cross Sectional Area of the Core → A
 Inductance (H) → L
 Length of the Core → ℓ

$$X_L = 2\pi f L$$

Supply Frequency (Hz) → f
 Inductive Reactance (Ω) → X_L
 Inductance (H) → L

$$L = \frac{X_L}{2\pi f} \quad \text{and} \quad f = \frac{X_L}{2\pi L}$$

Series Circuits	Parallel Circuits	Time Constant
$L_T = L_1 + L_2 + L_3 \dots$ $X_{L_T} = X_{L_1} + X_{L_2} + X_{L_3} \dots$	$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} \dots$ $\frac{1}{X_{L_T}} = \frac{1}{X_{L_1}} + \frac{1}{X_{L_2}} + \frac{1}{X_{L_3}} \dots$	$t = \frac{L}{R}$

Capacitance and Capacitive Reactance

$$Q = C \times V$$

Charge in Coulombs → Q
 Capacitance in Farads → C
 Volts across Capacitor → V

$$X_C = \frac{1}{2\pi f C}$$

Capacitive Reactance (Ω) → X_C
 Supply Frequency → f
 Capacitance (H) → C

$$C = \frac{1}{2\pi f X_C}$$

Capacitance (H) → C
 Supply Frequency (Hz) → f
 Capacitive Reactance (Ω) → X_C

Series Circuits	Parallel Circuits	Time Constant
$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \dots$ $X_{C_T} = X_{C_1} + X_{C_2} + X_{C_3} \dots$	$C_T = C_1 + C_2 + C_3 \dots$ $\frac{1}{C_{T_T}} = \frac{1}{X_{C_1}} + \frac{1}{X_{C_2}} + \frac{1}{X_{C_3}} \dots$	$t = R \times C$